

Audio Spectrum Analyzer


Team Members

Joseph Thompson and Jonathan Wimer

Introduction



Our Project:

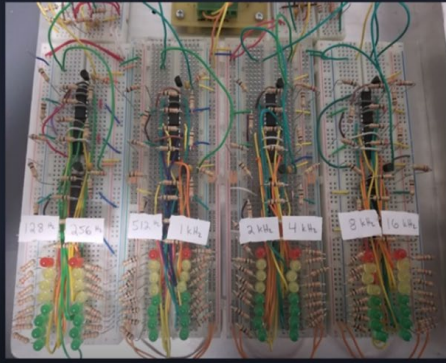- Audio Spectrum Analyzer ("Visualizer")
- Measures the magnitude of an input audio signal
 - Ours is electrical, some use acoustic pressure or even optical
- Use in industry by audio engineers to measure their work
 - Shows volume level of frequency bands, allows for visual feedback
- Ours is a simplified version
 - Educational and entertainment





LED Display

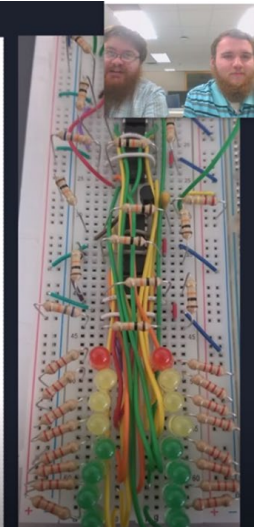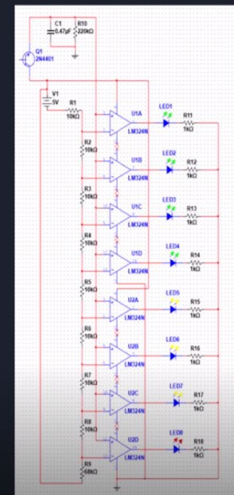- 8 x 8 LED matrix with colors representing magnitude of signal
- Transistor circuit boosts signal a bit more to drive LEDs
- LM324N chip used
 - Quad Op-Amp package
 - Popular general use chip, useful for our project
- Voltage divider circuit
 - Bottom green LEDs require less voltage to turn on compared to top red



Amplifier

- LM386 - general low voltage audio amp
 - Max gain of 200
- Upgraded circuit from original design
- Most important part
 - Maintain signal clarity to filters for accurate reading
- Capacitors are added to the power rail
 - Filter low and high frequency noise
- 0.1 uF capacitor added for extra decoupling to the chip
- 10k and 10uF capacitor added to decouple the input signal
- Adds a 470 pF capacitor to filter radio interference

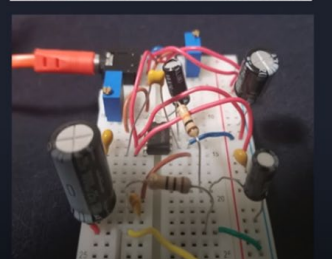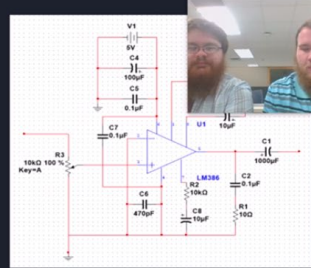


Final Project

- Completed on breadboards
- Signal flows from audio amplifier to bandpass filters to the LED display
- Amplifier increases input signal voltage
- Filters clip frequencies that are above and below desired frequency
- Display turns on LEDs according to output band pass signal
- "Dances" as music is applied




Amplifier Cont.

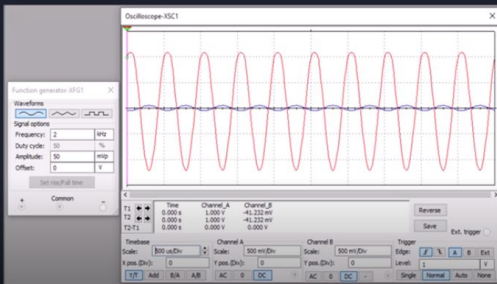
- Multisim simulation vs. Actual measurement



Final Project

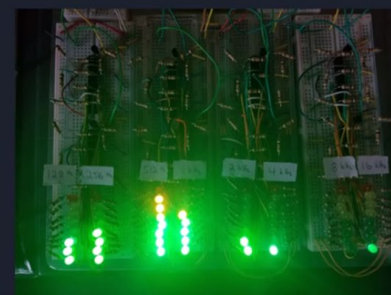

• 500 Hz tone input

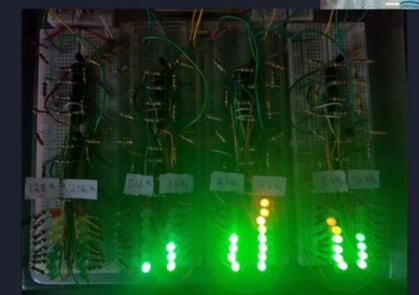

• 4 kHz tone input

Filters



- 8 active wide bandpass filters were used
 - Low "Q" factor
 - 128 Hz - 16 kHz
- Low pass and high pass filters cascaded together to filter desired frequency
- Op amp provides extra voltage gain and isolation to the circuit
- Equations:

$$f_{\text{upper}} = 1 / (2\pi R_1 C_1)$$

$$f_{\text{lower}} = 1 / (2\pi R_2 C_2)$$

$$f_{\text{center}} = \sqrt{f_{\text{upper}} * f_{\text{lower}}}$$
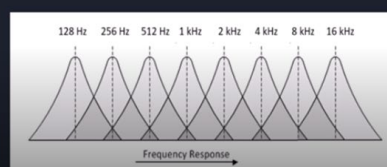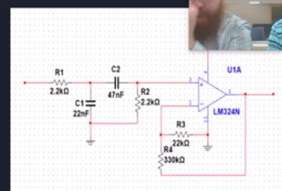
$$BW = f_{\text{upper}} - f_{\text{lower}}$$



Possible Improvements

- Automatic gain / volume control for input
 - Won't have to adjust each time
- More filters could be used with higher quality and narrower bandwidth
- More LEDs could be added to each band for more precise magnitude measurement



Conclusion

- Final project works as intended
- Completed 95% of objectives
 - Decreased overall size from 10 x 10 to 8 x 8
- Happy with the results
- Building on breadboards turned out to be positive
 - Will continue to work on in the future

